

**Phy335, Unit 3**  
**Diode circuits and DC Power**

**Mini-lecture topics planned:**

- **Metals and semiconductors**
  - **p-n junctions**
  - **DC power supply, ripple**
1. Measure the diode I-V from  $-15\text{ V}$  to about  $+0.6\text{ V}$  (apply forward voltage with caution).
  2. Design and test a diode-based asymmetrical clamp (also called “clipping circuit”) to limit the upper value of the input voltage to  $+5.6\text{ V}$ . Use the output from the signal generator (SG). [Typically, one clamps all non-zero voltages in a circuit for protection.] How would you add to this circuit to also clamp the lower value of the input at  $-5\text{ V}$ ? Draw the circuit in your lab report (assume you have an additional power supply of any voltage you choose).
  3. Design and build a full-wave rectifier to deliver  $20\text{ V DC}$  with less than  $0.5\text{ V}$  ripple using a  $165\text{ V AC}$  transformer output. Choose the capacitor and the “bleeder” resistor. Test this rectifier on the scope.