

## Op Amp Feedback and Effective Gain

For the Op Amp circuit with no feedback, like that one shown in Fig. 1, the output voltage  $v_{out}$  is given by the expression

$$v_{out} = g^{OL}(v_+ - v_-). \quad (1)$$

Over a wide frequency range, the open loop gain is  $g^{OL} = O(10^6)$ . For typical rail voltages  $V_{CC+}$  and  $V_{CC-}$  of 15 V, the maximum usable input difference  $(v_+ - v_-)$  is therefore limited to  $15 \text{ V}/g^{OL} = 15\mu\text{V}$ .

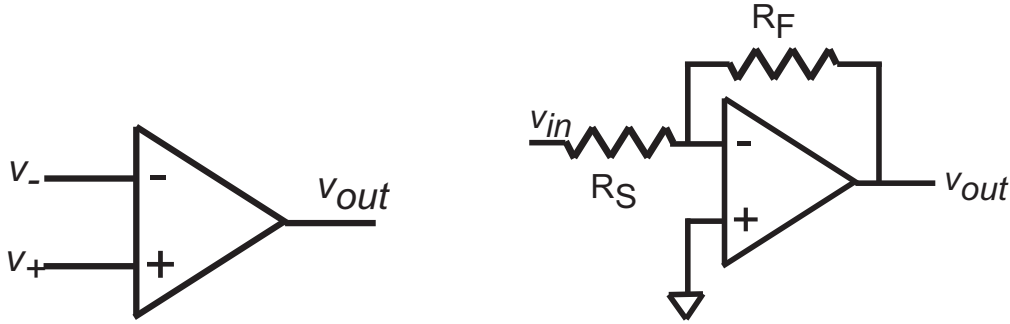


Figure 1: Op Amp circuit without feedback. Figure 2: Op Amp circuit with feedback.

However, adding *negative* feedback makes the (closed loop) voltage gain  $g \equiv v_{out}/v_{in}$  controllable by external components. For the circuit shown in Fig. 2, and using the high input impedance of an Op Amp so that  $i_+ = i_- = 0$ , one finds the equations governing the currents and voltages in the resistors to be

$$\begin{aligned} v_{out} &= g^{OL}(0 - v_-) \\ i_s &= \frac{v_{in} - v_-}{R_S} \\ i_f &= \frac{v_{out} - v_-}{R_F} \end{aligned}$$

where the first line comes from the Op Amp basic definition, the second and third are simply from Ohm's Law, and  $v_+ = 0$  because it is connected to ground. Because  $i_s = -i_f$  and  $v_{out} = g^{OL}v_-$ ,  $v_-$  can be eliminated from the above equations:

$$\begin{aligned} i_s &= -i_f \\ \frac{1}{R_S} \left( v_{in} + \frac{v_{out}}{g^{OL}} \right) &= \frac{-1}{R_F} (v_{out} g^{OL}) \\ \frac{1}{R_S} v_{in} &= - \left( \frac{1}{g^{OL} R_S} + \frac{1}{g^{OL} R_F} + \frac{1}{R_F} \right) v_{out} \end{aligned}$$

(continued on back)

and since  $g^{OL}R_S \gg R_F$  and  $g^{OL}R_F \gg R_F$ , the last line becomes

$$\frac{1}{R_S}v_{in} = -\frac{1}{R_F}v_{out}$$

which is trivially rearranged to become

$$g \equiv \frac{v_{out}}{v_{in}} = -\frac{R_F}{R_S}. \quad (2)$$

Back substitution then shows that  $v_- = 0$  which gives rise to the second golden rule  $v_+ = v_-$  (which we did not use, but derived).