

## Unit 6: Elements of Digital Electronics

Xueqi Li\*  
(Dated: Apr 28, 2018)

### INTRODUCTION

#### Binary

To change a number to binary or to convert back to decimal, one can use following equation:

$$\begin{aligned} & (B_n B_{n-1} \cdots B_2 B_1 B_0)_2 \\ & := \sum_{i=0}^n B_i 2^i = \sum_{i=0}^k D_i 10^i \\ & =: (D_k D_{k-1} \cdots D_2 D_1 D_0)_{10} \end{aligned} \quad (1)$$

On the other hand, for any base- $n$  to base- $m$  numeral system:

$$\begin{aligned} & (N_a N_{a-1} \cdots N_2 N_1 N_0)_2 \\ & := \sum_{i=0}^a N_i n^i = \sum_{i=0}^b M_i m^i \\ & =: (M_b M_{b-1} \cdots M_2 M_1 M_0)_{10} \end{aligned} \quad (2)$$

For example, if one wants to convert  $(137)_{10}$ , using Equation 2, one can find following:

$$\begin{aligned} & (137)_{10} \\ & = 1 \times 10^2 + 3 \times 10^1 + 7 \times 10^0 \\ & = 1 \times 2^7 + 1 \times 2^3 + 1 \times 2^0 \\ & = (10001001)_2 \end{aligned}$$

On the other hand, if one wants to convert  $(100101)_2$  to decimal, using Equation 2, one can obtain:

$$\begin{aligned} & (100101)_2 \\ & = 1 \times 2^5 + 1 \times 2^2 + 1 \times 2^0 \\ & = 3 \times 10^1 + 7 \times 10^0 \\ & = 37 \end{aligned}$$

#### Logic and Truth Table

It is well-know that from logic equation to truth table, one can just plug in all possible input, and calculate the output. On the other hand, one may wants to convert a truth table into logic equation. To do so, one can chose each output 1 line from the truth table, and add (or) them up.

For example, a selector have  $n$  input, and  $\log_2(n)$  select input. The select input select the input to be the output.

A	B	X	Y	O
1	0	0	1	1
1	1	0	1	1
0	0	0	1	0
0	1	0	1	0
0	1	1	0	1
1	1	1	0	1
0	0	1	0	0
1	0	0	0	0

TABLE I: Truth table of a 2 selector. A,B are input; X,Y are select input

For example, a 2 selector have truth table as Table I. We can chose the output 1 one and add them, Thus we have

$$O = A\bar{B}\bar{X}Y + AB\bar{X}Y + \bar{A}BX\bar{Y} + ABX\bar{Y}$$

#### Transistor-transistor Logic

In TTL system, the binary number can be present as high or low voltage. In ideal case, 0V is low and 5V is high. However, in real world, it is not possible to always obtain a 5V or 0V voltage. Thus, for TTL standard, any input higher than 2V is high, and any input lower than 0.8V is low. On the other hand, any output 3.5V is high and any ouput 0.5V is low.

#### Logic Gate

A logic gate accept some inputs and gives an output. The logic gate's truth table is same as mathematical logic. In the lab, we use NOT, AND, NAND, OR, NOR, XOR, and XNOR gate. The truth table is given in the appendix.

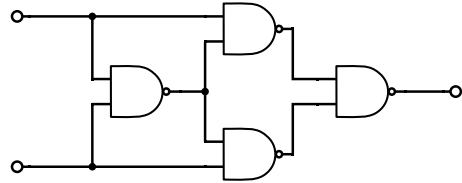


FIG. 1: Form a XOR gate using NAND gate

One can use NAND gate to form any other logic gate. For example, Figur 1 present how to form a XOR gate from NAND gate. The truth table is in the appendix.

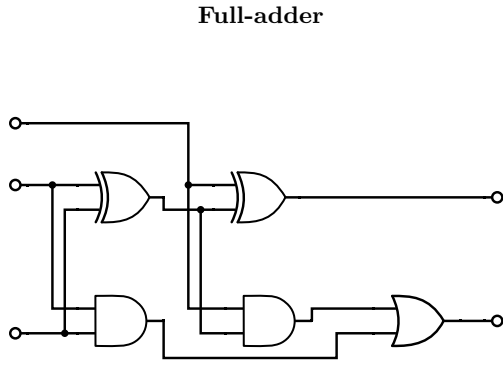


FIG. 2: A full-adder

One important application of logic gate is full-adder, presented in Figure 2, where the left side is input and the right side is output. The output of a full-adder is the result of binary addition of the input.

#### Two Bit Half-addder

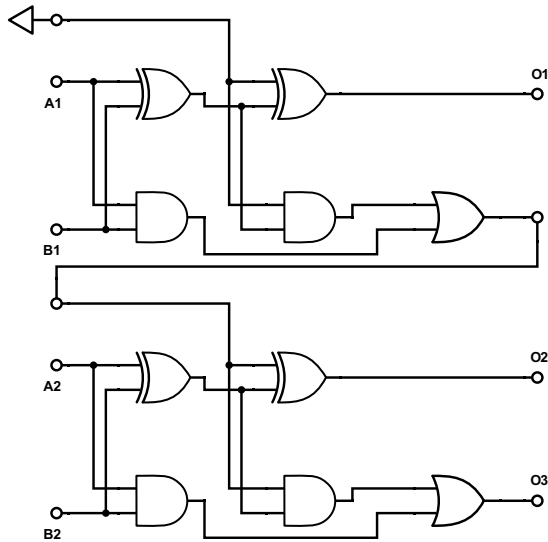


FIG. 3: A Two Bit Half-addder

Once obtain a full-adder, one can use full-adder to form a higher bit adder. For example, one can obtain a two bit half-addder as in Figure 3

#### Flip-flop

A Flip-flop, shown in Figure 4, can output one or zero when input are different and hold the output when the output are zero. There are a few applications of flip-flop.

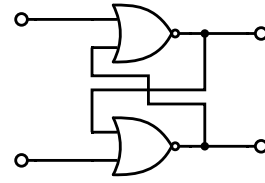


FIG. 4: A Flip-flop

#### Clocks

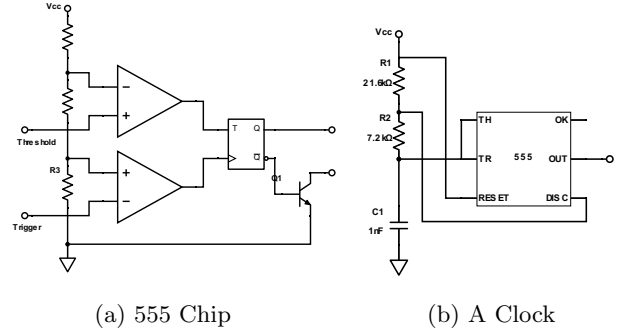


FIG. 5: An application of flip-flop

A nice application of flip-flop is clock. The key of the clock is the 555 chip, which is an application of flip-flop. The circuit of a 555 chip is present in Figure 5a, where all resistors are  $5k\Omega$ . The 555 chip divides  $V_{CC}$  into 3 parts, when the trigger voltage is larger than  $1/3 V_{CC}$  and the threshold voltage is smaller than  $2/3 V_{CC}$ , the output is hold, otherwise the output is 1 or 0 if the trigger voltage is below  $1/3 V_{CC}$  or the threshold voltage is higher than  $2/3 V_{CC}$ .

Then the clock is present in Figure 5b. This circuit can let the voltage periodically output zero or one, depending on the RC circuit. Thus, by calculating the voltage in the capacitor, one can find the period of the circuit.

$$\begin{aligned}
 V_C &= V_{CC}(1 - e^{-\frac{t}{RC}}) \\
 \Rightarrow t_{\text{high}} &= (R_1 + R_2)C \ln(2) \\
 t_{\text{low}} &= R_2 C \ln(2) \\
 \Rightarrow T &= (R_1 + 2R_2)C \ln(2)
 \end{aligned}$$

The duty cycle is how much time the voltage output is high:

$$\frac{t_{\text{high}}}{T} = \frac{R_1 + R_2}{R_1 + 2R_2}$$

For example, if one wants to have a 40kHz frequency clock with a 80% duty cycle, by the above equation, one can use a  $2.164k\Omega$  and  $7.213k\Omega$  resistors and a  $1nF$  capacitor, as the value shown in Figure 5b.

### **Clock Edge**

Another example of using flip-flop is D Clock Edge.  
The D flip-flop accepts a clock inputs.

### **DATA AND CALCULATION**

### **ANALYSIS**

### **CONCLUSION**

---

\* Partner: Tianming Hai