

Unit 1: Instruments, Signals, Resistors

Xueqi Li*
(Dated: Feb 10, 2019)

INTRODUCTION

Digital Multi-meters

The digital multi-meters is used when one want to measure the resistance, current, or voltage. It has buttons to switch to different function to measure different quality, and use another set of buttons to change the maximum value can be measure (and the unit sometime). To appropriately plug it into the circuit, different port on the multi-meters might be used. For our case, resistance and voltage share same port but current use a different port with two different maximum acceptable current. Once plugging into the circuit, One may read the digit on the screen of the meters to find the value of resistance, current, or voltage. It is important to make sure the current is smaller than the maximum acceptable current of the meters. For unknown current, usually use the larger maximum port first.

Root Mean Square

When measure a changing voltage with the voltagemeter mode. The meter gives a root mean square value:

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_t^{t+T} [V(t)]^2 dt}$$

For example, when giving a sine wave ($V(t) = V_0 \sin(\omega t)$), the reading would be $\frac{V_0}{\sqrt{2}}$. When giving a triangle wave in a amplitude of V_0 , the reading would be $\frac{V_0}{\sqrt{3}}$. And the reading of square wave would be its original amplitude.

Oscilloscope

A oscilloscope is used when measure the voltage. The oscilloscope can output a plot of voltage versus time so that one may identify the changes of voltage. To use a oscilloscope, one may plug two channel in to the circuit to measure the voltage of two different parts of the circuit. Once the scope been appropriately plugged into the circuit, one may use knobs on the scope to change the scale and position of the plot. Once the plot has been appropriate display on the screen, a measure button might be useful to read the accurate value of voltage, frequency, or other useful quality. One may use a the dual mode under

the display menu to display a plot of voltage of channel 1 versus voltage of channel 2.

Usually the oscilloscope measure function can give you the maximum value of the input voltage.

Signal Generator

A signal generator is used when the input voltage is required to be a sine wave, a square wave, or a triangle wave. One can use the form button to change between those wave form. To change the frequency, use the numberpad and the unit button. It is also possible to change the amplitude by using the amplitude knobs.

Grounded

An important principle of using those devices is to notice that the outer shell is connected to the ground. Thus, the outer shell of different devices are connected together. It is a good idea to keep all outer shell connect at the same point of the circuit so that it does not affect the circuit.

Jobboard

The board is useful to connect the circuit. The board which is used in this lab have two different layout. The first one is the long panel where the width is two port. Such panel connected the port in column together and marked as red and blue lines. The other one have width as five port. Such panel connected the port in rows together.

One may use wires and ohmmeter to identify which of two ports are connected. The open circuit gives the meter no reading (blinking zero), and the connected ports will give meter a small reading.

One may use wire stripper or pre-cut jumpers to help the layout of the circuit on the board. To use the wire stripper, one can cut the wire or strip the insulation shell of the wire. A pre-cut jumpers can be used to connect different part of the board into one.

Resistor Bar Code

A resistor bar code can give useful information of the resistor such as its resistance. One may refer to Table I to find its resistance.

Color	Significant digits	Multiplier
Black	0	10^0
Brown	1	10^1
Red	2	10^2
Orange	3	10^3
Yellow	4	10^4
Green	5	10^5
Blue	6	10^6
Violet	7	10^7
Grey	8	10^8
White	9	10^9

TABLE I. Color code for resistance value

Resistor

A resistor follows Ohm's law linearly:

$$R = \frac{V}{I}$$

If we connect two resistor in series, they would share same current but occupied different voltage. One may find:

$$R_{\text{total}} = R_1 + R_2$$

If we connect two resistor in parallel, they would share same current but use different current. One may find:

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Ohmmeter

The lab is using a GDM-8145 multi-meter. When using as a ohmmeter, it will apply 0.2V or 2V on the resistor[1]. The current passed through the resistor is given as $I = \frac{V}{R}$.

Ohm's Law

A conductor usually have some electric conductivity:

$$\sigma = \frac{1}{\rho}$$

Where ρ is resistivity of the material. Usually the conductivity is a constant, this imply the Ohm's law:

$$\vec{J}(\vec{r}) = \sigma \vec{E}(\vec{r})$$

Thus, one may find the current:

$$I = \int \vec{J} \cdot d\vec{A}$$

where the integral is over the cross section. One may also find the voltage as:

$$V = - \int \vec{E} \cdot d\vec{l}$$

This give us the resistance:

$$R := \frac{V}{I}$$

Measuring Resistance with a Scope

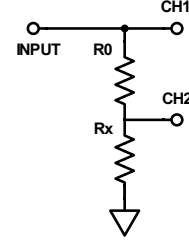


FIG. 1. Circuit of resistance measurement

One may measure the resistance of a resistor by using circuit in Figure 1. Where R_0 is some knowing resistor with a large resistance. To find the resistance, one may wish to find the current and the voltage on the unknow resistor. Here, channel 1 measure the current:

$$I = \frac{V}{R_{\text{total}}} = \frac{V}{R_0 + R_x} \approx \frac{V}{R_0}$$

This approximation is able to use since R_0 is much larger than R_x

Once the current is found, one can calculate the resistance:

$$R = \frac{V_{\text{CH2}}}{I} = \frac{V_{\text{CH2}} R_0}{V_{\text{CH1}}}$$

It is easy to see that the a plot of voltage of channel 2 versus voltage of channel 1 is useful, One may use the dual mode of the scope to output such plot and find $\frac{V_{\text{CH2}}}{V_{\text{CH1}}}$ as the slope.

Voltage Divider

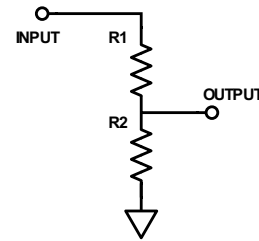


FIG. 2. A voltage divider

A voltage divider is form by the circuit of Figure 2. One may find the current is given as:

$$I = \frac{V_{in}}{R_{total}} = \frac{V_{in}}{R_1 + R_2}$$

Thus, the voltage on R_2 , which is also the output voltage, is given as:

$$V_{out} = V_2 = IR_2 = \frac{V_{in}R_2}{R_1 + R_2}$$

Thus, one may also find from above equation

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

For example, to have a 1 : 10 divider, it is nesseary to have $R_1 = 9R_2$. To have a 1 : 5 divider, it is nesseart to have $R_1 = 4R_2$

Voltage Divider and Other Device

Many device have a build-in resistor. Thus, when using them with other resistor, sometimes it forms a voltage divider and affect the measurement. For example, the signal generator in lab have a 50Ω build-in resistor. It is nesseary to use a large resistor in the circuit to avoid the influences of the build-in resistor.

Decibel Unit

The Decibel (dB) is a logarithmic unit defined by:

$$G_{dB} = 20 \log_{10}(\frac{V_0}{V})$$

For example, if given V_0 as 1V, than 1V is 0dBV, 10V is 20dBV, 1mV is -60dBV.

Thevenin's equivalents

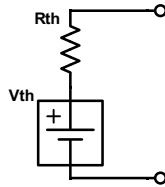


FIG. 3. Thevenin's equivalents

Thevenin's theorem suggest that any linear electrical circuit with voltage sources and resistances have a equivalent circuit with one voltage sources and one resistor in series as present in Figure 3. One may construct such

equivalent circuit by finding the equivalent voltage V_{th} and the equivalent resistor R_{th} .

To find the equivalent voltage and resistor, one can measure the voltage and the current of the output of the circuit. The equivalent voltage is juat as same as measured voltage and the equivalent resistor can be find by Ohm's law as $R_{th} = \frac{V}{I}$. However, it is not safe to direct plug the ammeter on the output since the output current might be very large and damage the ammeter. One may use a load resistor parallel with a voltmeter to find the equivalent resistor. Consider the whole circuit as a voltage divider, the output of the voltmeter follows equation:

$$V = \frac{V_{th}R_L}{R_{th} + R_L}$$

Thus we can find the equivalent resistor have resistance as:

$$R_{th} = \frac{V_{th}R_L}{V} - R_L$$

DATA

DC Power

One may measure the voltage of a DC power supply. The reading from the DMM is $5.05 \pm 0.01V$, and the reading from oscilloscope is $5.02 \pm 0.25V$.

Resistor

Resistor	Code bar [Ω]	Measurement [Ω]	Difference
R_1	3.3×10^4	$3.35(1) \times 10^4$	1.52(1)%
R_2	1.0×10^3	$1.10(1) \times 10^3$	10.00(1)%
R_3	1.10×10^4	$1.106(1) \times 10^4$	0.54(1)%

TABLE II. Code bar reading and the real value

A resistor might have different resistance from its bar code. Please find the measument and the bar code reading in the Table II.

One can also form a circuit to connect those resistor in series, parallel, and series-parallel as in Figure 4. We can

Circuit	Theoretical [Ω]	Measurement [Ω]
Series	$4.57(5) \times 10^4$	$4.60(1) \times 10^4$
Parallel	$9.71(1) \times 10^2$	$9.72(1) \times 10^2$
Series-parallel	$1.17(10) \times 10^4$	$1.21(1) \times 10^4$

TABLE III. Series or parallel of resistor

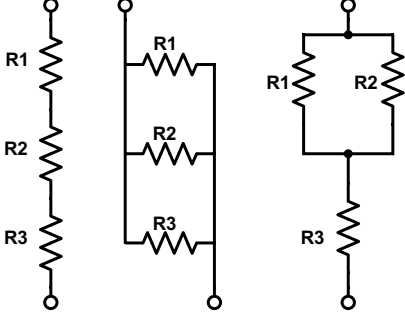


FIG. 4. Series, parallel, and series-parallel from left to right

measure the resistance in each case as in Table III. To find the theoretical value of the resistor, we can proceed following computation:

1. Series:

$$R = R_1 + R_2 + R_3 = 4.57 \times 10^4 \Omega$$

$$\sigma_R = \sqrt{\sum \left(\frac{\partial R}{\partial R_i} \right)^2 \sigma_{R_i}^2} = 0.05 \times 10^4 \Omega$$

2. Parallel:

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 9.71 \times 10^2 \Omega$$

$$\sigma_R = \sqrt{\sum \left(\frac{\partial R}{\partial R_i} \right)^2 \sigma_{R_i}^2} = 0.01 \times 10^2 \Omega$$

3. Series-parallel:

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} + R_3 = 1.17 \times 10^4 \Omega$$

$$\sigma_R = \sqrt{\sum \left(\frac{\partial R}{\partial R_i} \right)^2 \sigma_{R_i}^2} = 0.10 \times 10^4 \Omega$$

By reconnected the resistor, we find the board connection have a small resistance.

Measure resistance using scope

To measure the unknown resistance as in the introduction, We use a load resistor with resistance $3.35(1) \times 10^4 \Omega$, and obtained a plot with slope of $k = \frac{0.15(1)V}{5.0(5)V} = 0.030(3)V$. Thus we have $R_x = kR_0 = 1.01(10)\Omega$. The real value of the resistor is $1.10(1) \times 10^3 \Omega$ by measurement.

Voltage divider

To achieve a 1:10 voltage divider, we use R_1 as three resistor in series to have a $5200\Omega + 3670\Omega + 150\Omega = 9020\Omega$

resistance, and we use a 1000Ω as R_2 . In measurement with a scope, we find the image coincide when we use the input channel in a scale of 1V and the output channel in a scale of 100mV. This is indeed a 1:10 voltage divider. The error is the half of the minimum scale (10mV). When apply a DC power of 15.00(1)V, we find the output is 1.49(1)V.

TABLE IV. Output and Input for voltage divider

Sine Wave Set 1		
Input Frequency	Output Voltage[mV]	Output Frequency
100Hz	204(4)	100.0(1)Hz
1kHz	204(4)	1.00(5)kHz
500kHz	200(1)	500(1)kHz
700kHz	192(4)	700(2)kHz
1MHz	176(4)	1.00(1)MHz
2MHz	128(4)	2.00(1)MHz
3MHz	92(4)	3.00(2)MHz
4MHz	72(4)	4.00(5)MHz
5MHz	56(4)	5.00(5)MHz
10MHz	28(4)	10.00(1)MHz

Sine Wave Set 2		
Input Frequency	Output Voltage[mV]	Output Frequency
100Hz	100(4)	100(2)Hz
1kHz	100(4)	1.00(3)kHz
5kHz	100(1)	5.00(1)kHz
1MHz	88(4)	1.00(2)MHz
5MHz	42(4)	5.00(5)MHz
9MHz	36(4)	8.95(5)MHz

Triangle Wave		
Input Frequency	Output Voltage[mV]	Output Frequency
100Hz	100(4)	100(2)Hz
1kHz	100(2)	1.00(2)kHz
5kHz	100(2)	5.00(5)kHz
1MHz	74(2)	1.00(5)MHz

Square Wave		
Input Frequency	Output Voltage[mV]	Output Frequency
100Hz	100(2)	100.0(3)Hz
1kHz	100(2)	1.00(5)kHz
5kHz	100(4)	5.00(5)kHz
1MHz	100(2)	1.00(2)MHz
5MHz	66(2)	5.00(3)MHz
9MHz	48(2)	9.0(1)MHz

^a The input voltage is 2V for each measurement on sine wave set 1. The input voltage is 1V for each of other measurement.

^b Two set of result of sine wave are perform in different date.

When using different frequency in the input from the signal generator, we obtained this result as in Table IV.

Signal Generator

When set the signal generator to 100Hz, we see the result on the scope is 100(2)Hz when they are connected directly.

Phase shift

Input	Time Difference [ns]	Phase Shift
1MHz	65.0(75)	0.498(5)
2MHz	77.5(75)	0.817(9)
3MHz	52.5(50)	1.225(14)

TABLE V. Phase shift of a voltage divider

One can measure the phase shift between the output and input of a voltage divider as in the Table V. To calculate the phase shift, we use $\Delta\varphi = \frac{\Delta t}{T} 2\pi$ where $T = \frac{1}{f}$. The phase shift before 500kHz is unrecognizable.

Root Mean Square

Waveform	Frequency	Scope[mV]	DMM[mV]
Sine	100Hz	204(4)	56(1)
Square	100Hz	212(2)	211(5)
Triangle	100Hz	200(1)	57(1)
Sine	1kHz	204(4)	57(1)
Square	1kHz	206(4)	230(1)
Triangle	1kHz	200(2)	57(1)
Sine	100kHz	208(4)	27(1)
Square	100kHz	220(4)	254(5)
Triangle	100kHz	200(4)	38(1)
Sine	1MHz	148(4)	57(1)
Square	1MHz	196(4)	507(1)
Triangle	1MHz	124(4)	58(1)

TABLE VI. Difference between maximum value and RMS value

One can measure the maximum value of a waveform by using a scope, or measure a RMS value using a DMM. A result is present in the Table VI

Decibels

The -20dB setting on the signal generator can change the amplitude. This setting will theoretically reduced the amplitude to its $\frac{1}{10}$ of original. A data obtained before and after using the dB setting is present in Table VII

Before[V]	After[mV]	Theoretical[V]
4.0(2)	400(4)	0.4
6.0(2)	720(4)	0.6
8.0(2)	1000(40)	0.8
10.0(2)	1200(40)	1.0

TABLE VII. Before and after change the dB setting

Thevenin's Equivalents

One can form a 1:2 voltage divider with a 15 V voltage sources and find its equivalent. By measurement, we find the output is 7.60(4)V and 14.9(1)mA, this give us the equivalent voltage as 7.60(4)V and the equivalent resistor is 510.07(5) Ω . We can calculate the theoretical equivalent resistor as following:

$$R_{th} = \frac{V_2}{I_{no2}} = \frac{R_2 I}{\frac{V_{in}}{R_1}} = \frac{R_2 \frac{V_{in}}{R_1 + R_2}}{\frac{V_{in}}{R_1}} = 500\Omega$$

$$V_{th} = V_2 = R_2 \frac{V_{in}}{R_1 + R_2} = 7.5V$$

Load Resistor

Load[k Ω]	Output Voltage[V]	$R_{th}[\Omega]$	Theoretical Voltage
50	0.680(1)	501(1)	0.682
500	3.75(1)	500(1)	3.75
5000	6.80(1)	514(1)	6.82

TABLE VIII. Load resistor and the output

One may also apply a load resistor to the output and find the equivalent resistor. A measurement is as Table VIII. To find the equivalent resistor, one can apply

$$R_{th} = \frac{V_{th} R_L}{V} - R_L$$

$$\sigma_{R_{th}} = \sqrt{\left(\frac{\partial R_{th}}{\partial R_L}\right)^2 \sigma_{R_L}^2 + \left(\frac{\partial R_{th}}{\partial V}\right)^2 \sigma_V^2}$$

Series and Parallel

One can use different resistors to form a series and parallel circuit. A such circuit is presented in Figure 5 with a input 15V DC. We can pick a output point and measure the equivalent circuit. In measurement, we find the voltage is 12.936(5)V and the current is 12.61(5)mA. We may refer it as Figure 3 to find the equivalent voltage is 12.936(5)V and the equivalent resistor is 1.025(6) $k\Omega$. The theoretical value of equivalent resistor can be calculate to be 1.009 $k\Omega$.

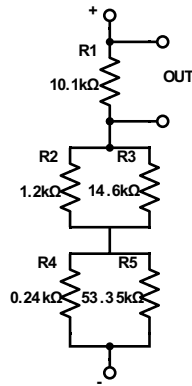


FIG. 5. Series and Parallel Resistors

ANALYSIS

DC Power

The result is reasonable. The DC power gives around 5V voltage and the result in DDM and scope agrees in 2σ .

Resistor

The result is reasonable. Most of the resistor have a less than 2% difference than its color bar. One resistor have difference in 10%. This resistor might needed to be replaced from the lab.

For series and parallel those resistor, the theoretical value and the measurement value are closed. The measurement value is a little bit larger than the theoretical value, that might be due to the resistor on wire.

Measure resistance using scope

The resulted value and the theoretical value agrees each other within 1σ .

Voltage divider

We do achieve a 1:10 voltage divider. We find that in high frequency, the output voltage dropped in all waveform, which is not as expected in theory. It is true that the maximum input voltage did not change, it might be the case that the resistance is not truly linear in high frequency, or some voltage might be expend when it translate in wire in high frequency.

Signal Generator

The signal generator is capable to generate asking frequency within 1σ .

Phase shift

For higher frequency, we see a phase shift in the output. Higher the frequency, higher the phase shift. It might be the case that the current have a delay since it takes time to transmit to the output channel.

Root Mean Square

The result is not reasonable. We see that in square wave, low frequency gives a reasonable result (RMS is equal to maximum). However, in high frequency, it does not gives a reasonable result. It might be the case that when high frequency, the signal generator cannot generate a well square wave sometimes. The wave form might be decompose into dispersed sin wave given by Fourier transform, thus it gives a none reasonable result. For sine and triangle wave, it does not gives reasonable result at all. As in the introduction part, the result of the sine wave should be $\frac{V_{\max}}{\sqrt{2}}$ and the result of the triangle wave should be $\frac{V_{\max}}{\sqrt{3}}$. There might be a operation error.

Decibels

The result is not very well. The result value is close to the theoretical value but higher. That might be a defect on signal generator.

Thevenin's Equivalent

The result is reasonable. The theoretical value and the resulted value are closed but the resulted value is higher. That might be due to the resistance of wire.

Load resistor

The result is reasonable. We see that the load resistor closed to the equivalent resistor gives more precise value.

Series and Parallel

The result is reasonable. The theoretical value and the resulted value are within 2σ .

One may ask for such circuit, how does the load resistor affect the result value. We can think such current

as a voltage divider (think R_2 , R_3 , R_4 , and R_5 as one resistor R_1 in voltage divider and the original R_1 is R_2 in voltage divider). One can find by direct measurement, the equivalent resistance can be found by

$$R_{Dth} = \frac{V_2}{I_{no2}} = \frac{V_{in} R_2}{R_1 + R_2} \frac{R_1}{V_{in}} = \frac{R_1 R_2}{R_1 + R_2}$$

However, when we use a load resistor, we can find

$$\begin{aligned} R_{Lth} &= \frac{V_{th} R_L}{V_L} - R_L \\ &= \frac{V_{in} R_2 R_L}{R_1 + R_2} \frac{R_1 + (\frac{1}{R_L} + \frac{1}{R_2})^{-1}}{V_{in}} \left(\frac{1}{R_L} + \frac{1}{R_2} \right) - R_L \\ &= \frac{R_2 R_L (R_1 + (\frac{1}{R_L} + \frac{1}{R_2})^{-1})}{R_1 + R_2} \left(\frac{1}{R_L} + \frac{1}{R_2} \right) - R_L \end{aligned}$$

Now we can see that the direct measurement is not dependent on anything but the loaded measurement is dependent on the load resistor. We can use the equation to

find when would the the the load resistor make the result have more error. After a calculation, even $1M\Omega$ is still within the 10% range for this circuit.

CONCLUSION

Overall the result is reasonable. However, the root mean square part has a serious error. This might be due to a operation error, or the wire connected to the DMM has some problem. In the last part, maybe it is necessary to view the equation in a log scale.

* Partner: Tianming Hai
 [1] *GDM-8145 User Manual*, Good Will Instrument Co., Ltd (2017).